
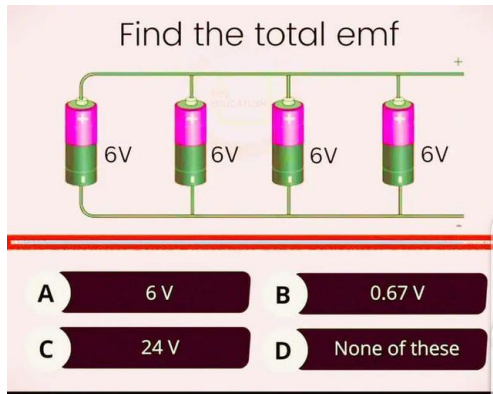


Basic Electronics

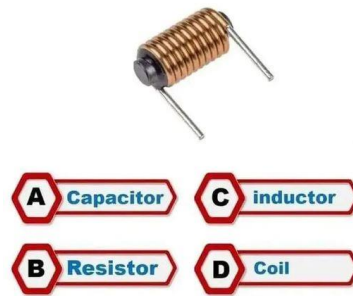

Ans- 6 V


Q2. What is this ?




Ans- Inductor




Ans- Wrong

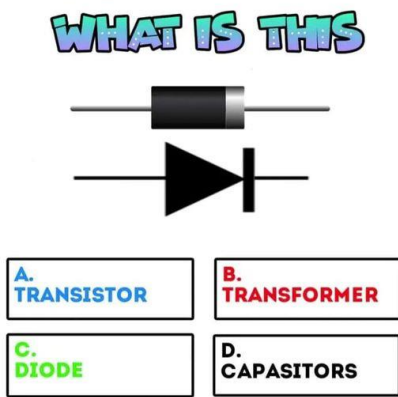


Ans- Diode

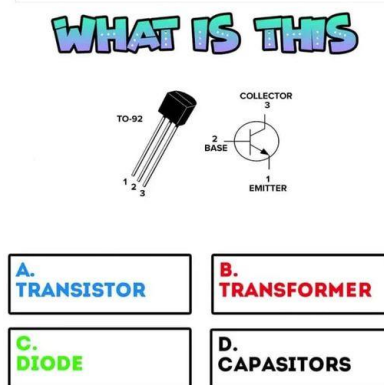


Ans- Transistor

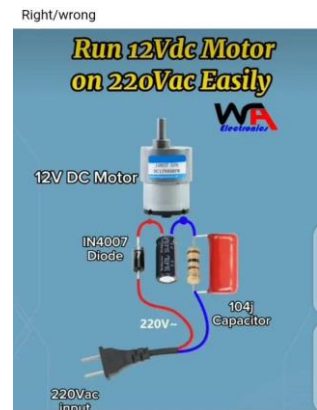

Ans- ?

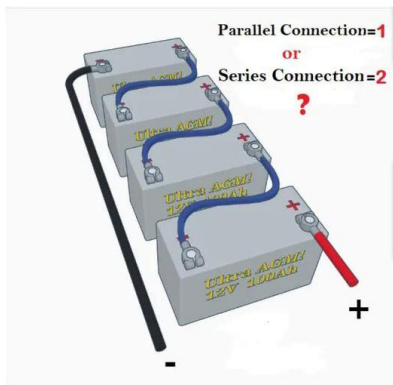


Ans- 2

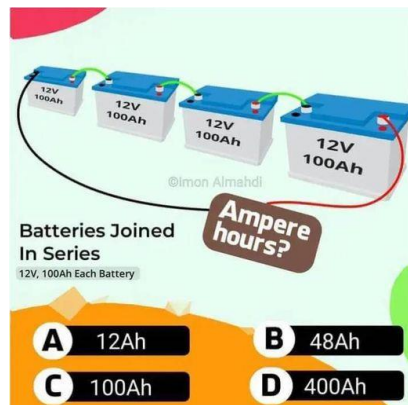


Ans-C

What is this ?



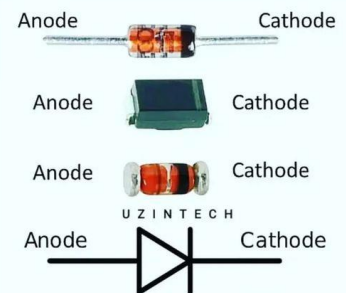


Ans- Diode

Right/wrong

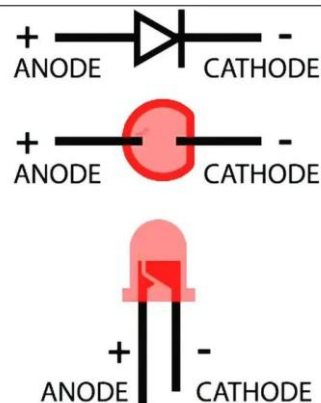

Ans- Right

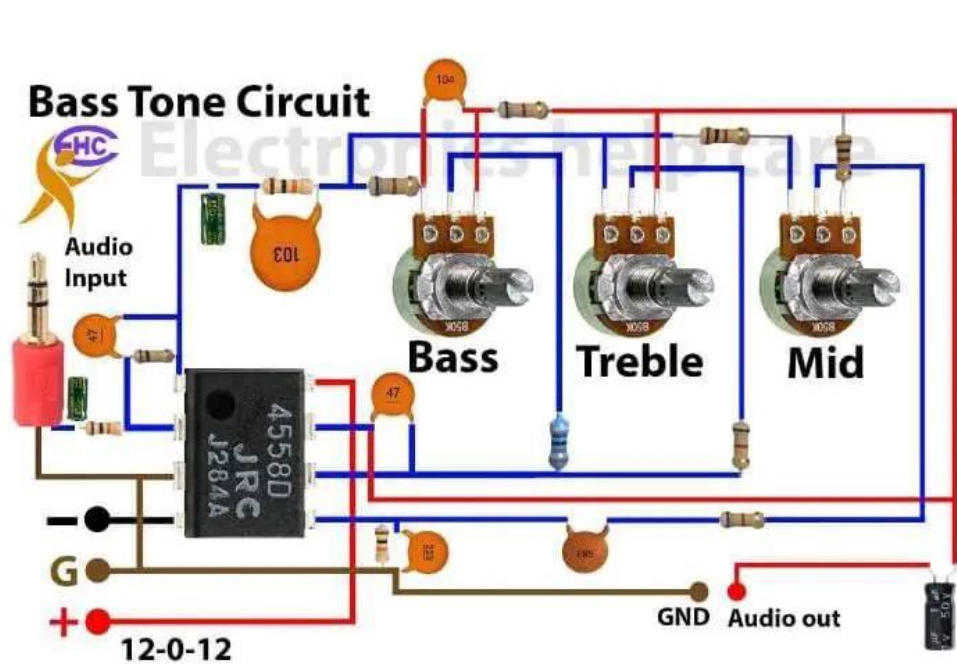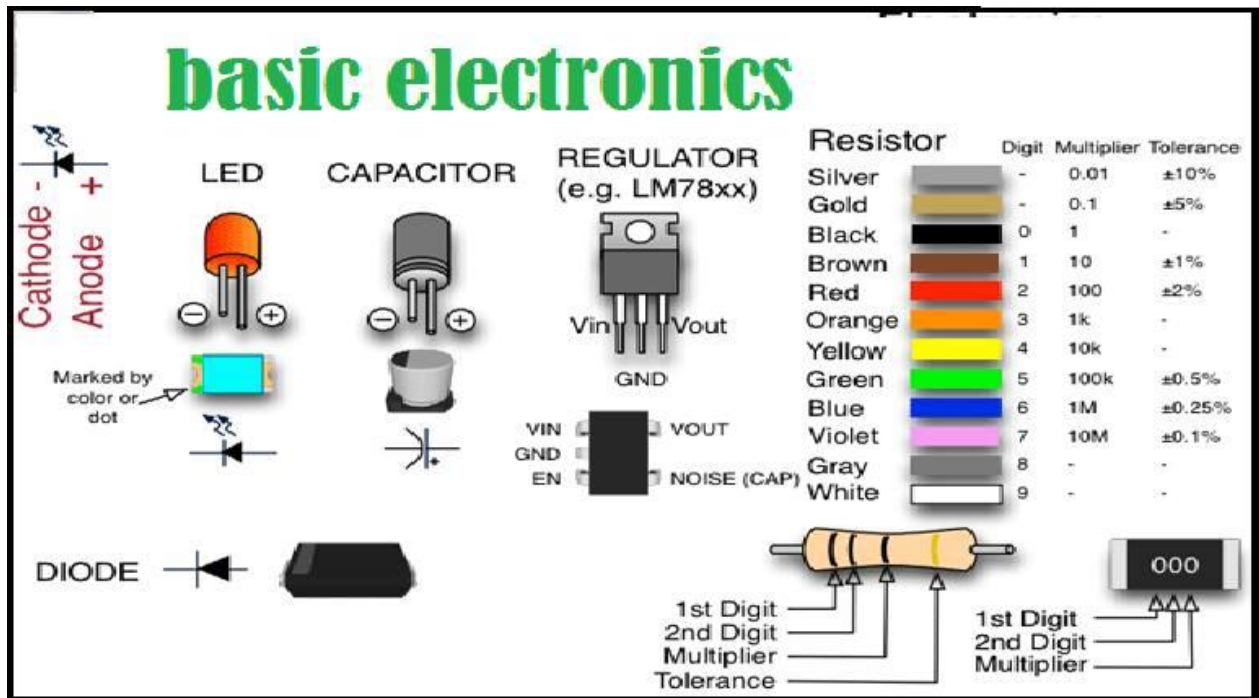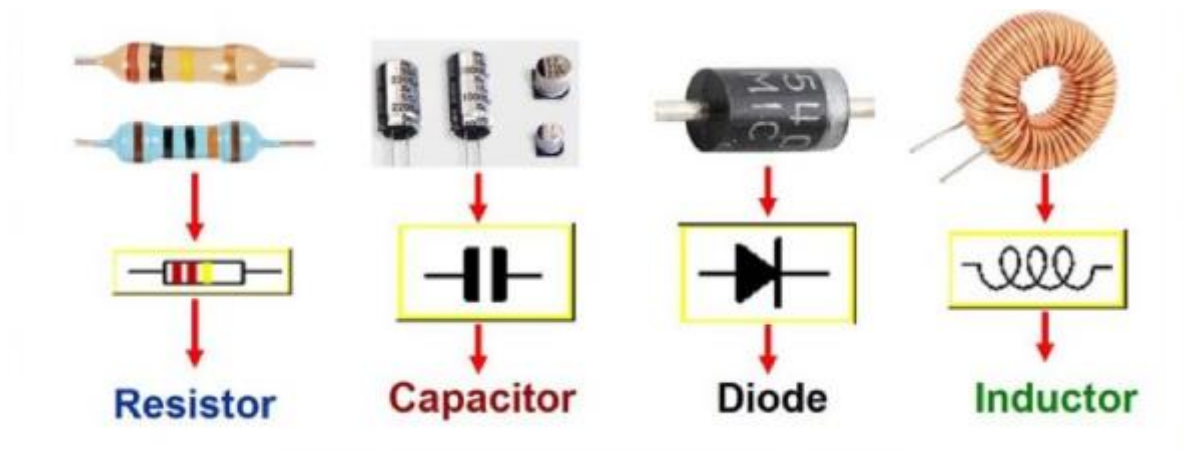

By- Dr. Vijay V. Warhate

M.Sc. Physics, B.Ed. UGC-SET, CSIR-NET (All India Rank-51), Ph.D.